University of British Columbia
Electrical and Computer Engineering
Electrical and Biomedical Engineering Design Studio
ELEC291/ELEC292

Adding WAV Sound to the PIC32MX130

Copyright © 2021, Jesus Calvino-Fraga. Not to be copied, used, or revised without explicit written permission from the copyright owner.
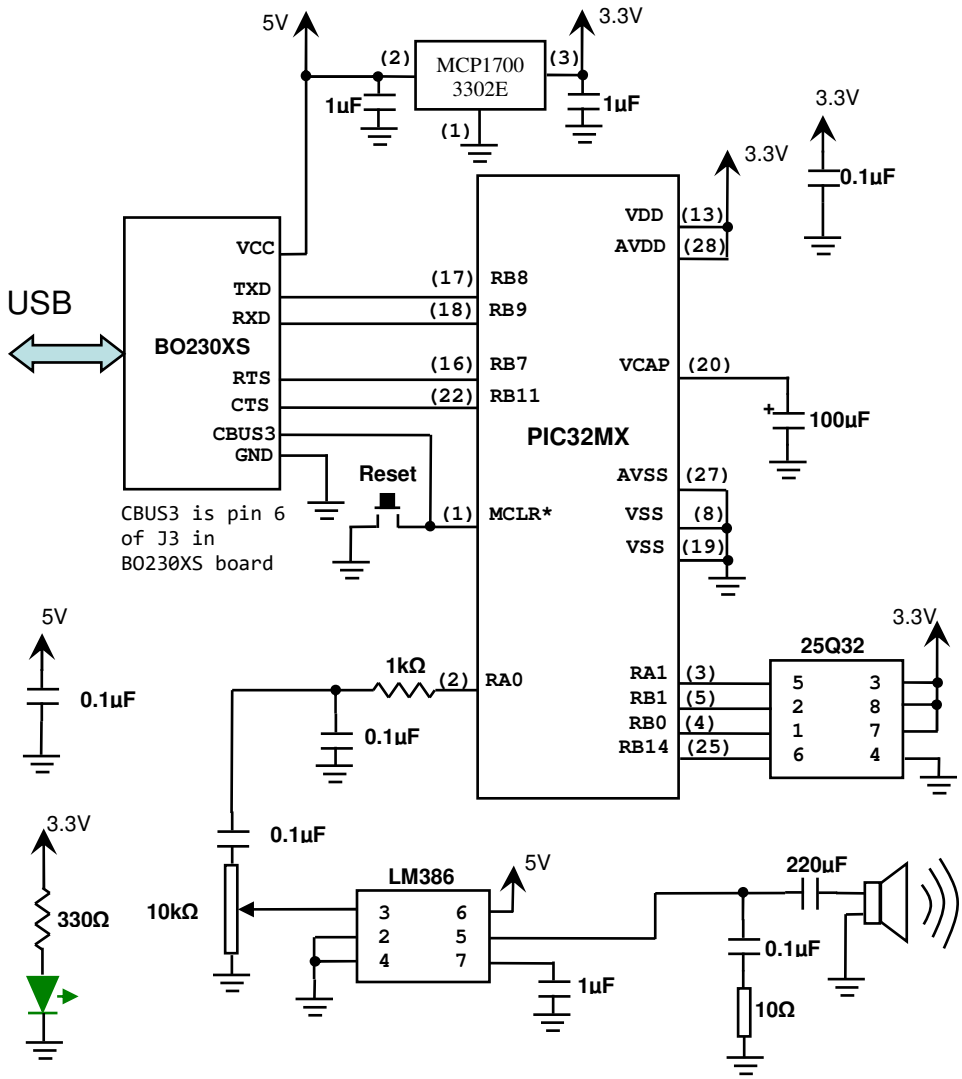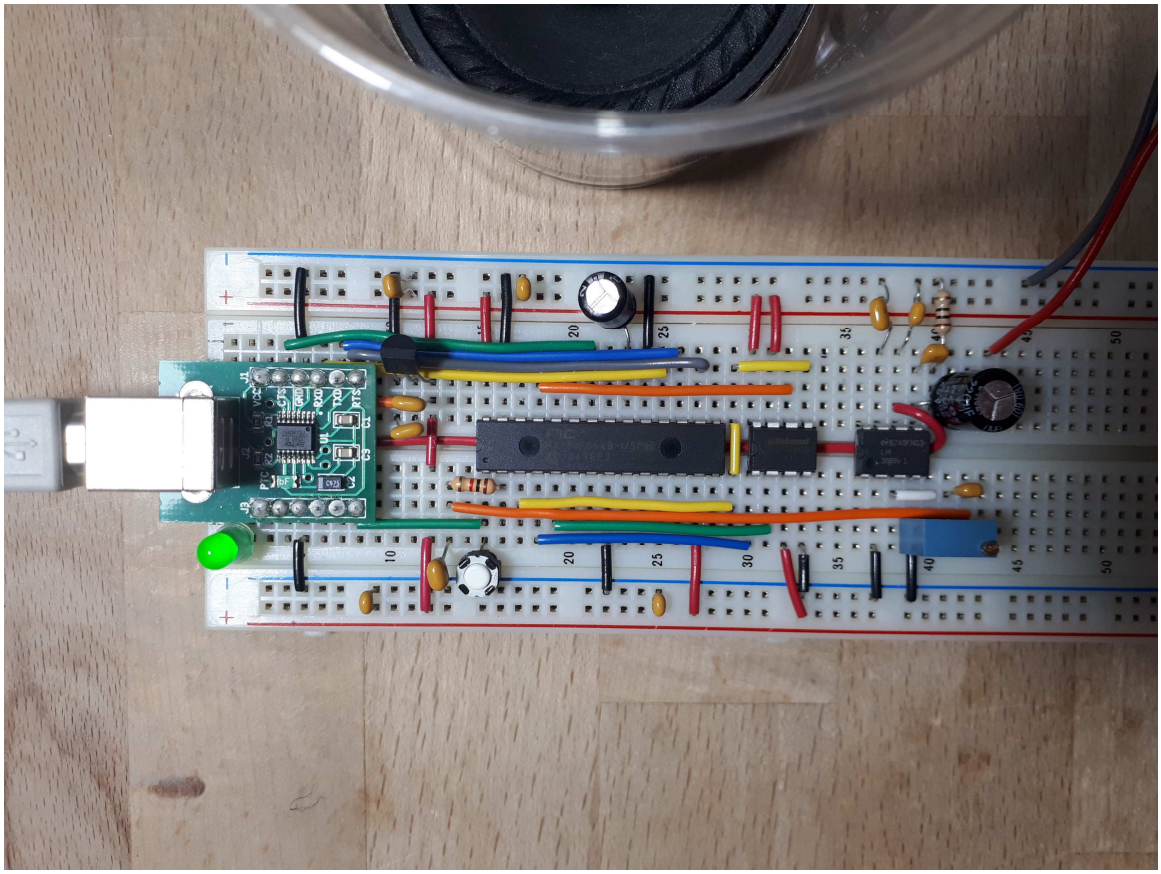
The diagram below shows the connections required to add WAV sound to the PIC32MX130 using PWM.